

$$R_1 = 0$$

$$V_+ = V_{S2} \approx V_-$$

$$\frac{V_{S2} - V_{S1}}{2\mu} + \frac{V_{S2} - V_o}{1\mu} \approx 0 \rightarrow V_o = \frac{3}{2} V_{S2} - \frac{1}{2} V_{S1}$$

$$V_{S2} = 4V_{S1} \rightarrow V_o = 5.5 V_{S1}$$

$$\Rightarrow |V_o| < 15 \rightarrow |V_{S1}| < \frac{15}{5.5}$$

$$|V_{S2}| < \frac{80}{5.5}$$

b)  $V_{S1} = 0$   
 $R_1 = 0$

$$KCL(1) : \frac{V_{S2} - 0}{2\mu} + \frac{V_{S2} - V_o}{1\mu} = 0 \rightarrow V_o = \frac{3}{2} V_{S2}$$



$$|V_{EE}| = 15 \quad \text{بفرض انتقال بودن مخرج حرجي}$$

$$V_o = 15 \quad \xrightarrow{\text{معادلة 1}} \quad V_- = \frac{2}{3} \times 15 = 10$$

$$V_+ - V_- > 0 \rightarrow V_{S2} - 10 > 0 \rightarrow V_{S2} > 10$$

$$V_o = -15 \rightarrow V_- = -10$$
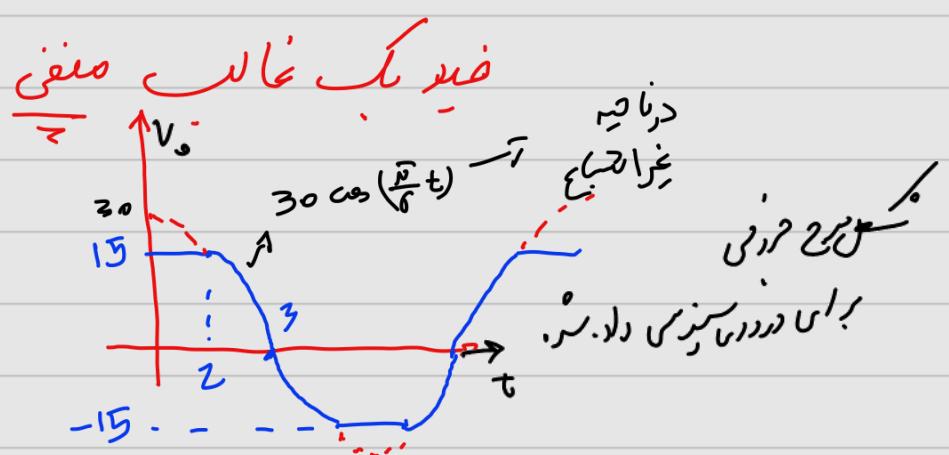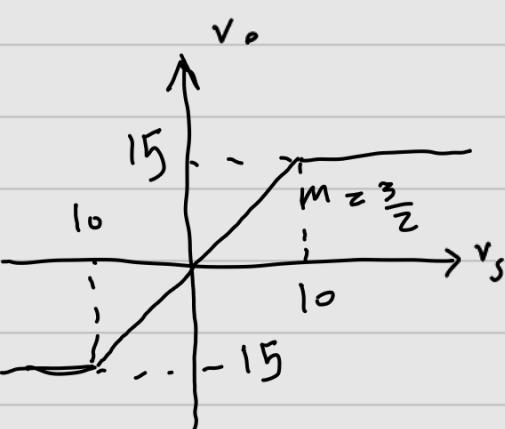
$$V_+ - V_- < 0 \rightarrow V_{S2} \leq -10$$



C)  $V_{S1} = 0, R_1 = 0$



$$V_- = V_{S2} \rightarrow \frac{V_{S2} - 0}{2\mu} + \frac{V_{S2} - V_o}{1\mu} \Rightarrow V_o = 1,5 V_{S2}$$

$$V_o = 15 \rightarrow V_t = 10 \quad , \quad V_- = V_{S2}$$


$$V_t - V_- > 0 \rightarrow V_{S2} < 10$$

$$V_o = -15 \rightarrow V_t = -10$$
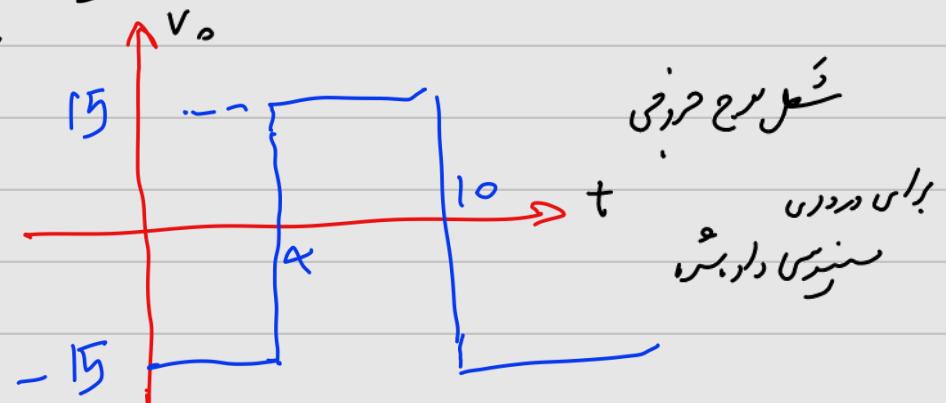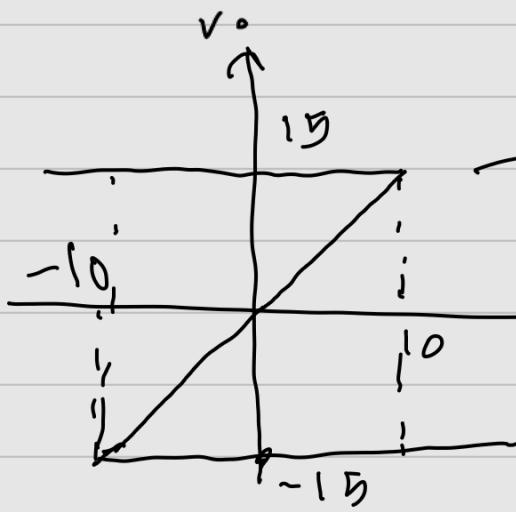
$$V_t - V_- < 0 \rightarrow V_{S2} > -10$$



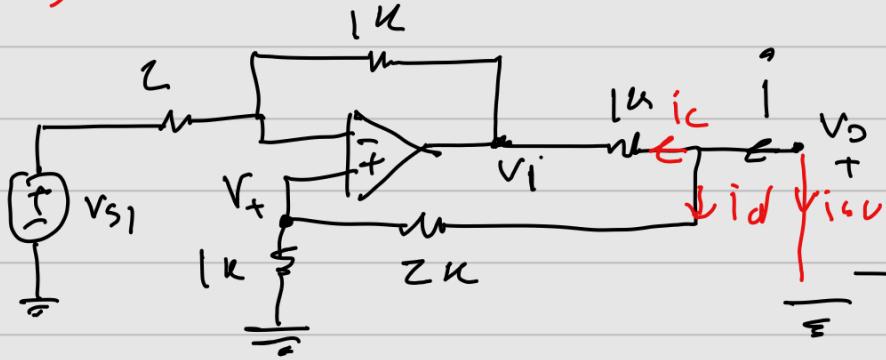d)  $V_{S2} = 0 \quad R_1 = 1 \text{ k}\Omega$



$$V_+ = \frac{1}{3} V_0 \quad (\text{معادلة مترافق})$$

$$V_- = V_+ = \frac{1}{3} V_0 \rightarrow \frac{\frac{V_0}{3} - V_{S1}}{2k} + \frac{\frac{V_0}{3} - V_i}{1k} = 0$$

$$V_i = \frac{V_0 - V_{S1}}{2}$$

$$i = \frac{V_0}{3k} + \frac{V_0 - \frac{V_0 - V_{S1}}{2}}{1k} = \frac{5}{6} V_0 + \frac{V_{S1}}{2}$$

$$\rightarrow V = \frac{6}{5} i - \underbrace{\frac{3}{5} V_{S1}}_{V_{OC}} \rightarrow i_{SC} = \frac{Z}{V_{OC}} = -\frac{1}{2} V_{S1}$$

$$V_0 = 0 \quad \text{لذلك} \quad V_0 = 0 \rightarrow i_d = \frac{0 - 0}{3k} = 0$$


$$i_{SC} = \frac{V_i}{1k} \rightarrow i_C = -i_{SC} = 0$$

برهان

$$V_+ = \frac{V_0}{3} = 0 \rightarrow \frac{0 - V_i}{1k} = \frac{V_{S1} - 0}{2k}$$

$$V_i = -\frac{V_{S1}}{2}$$
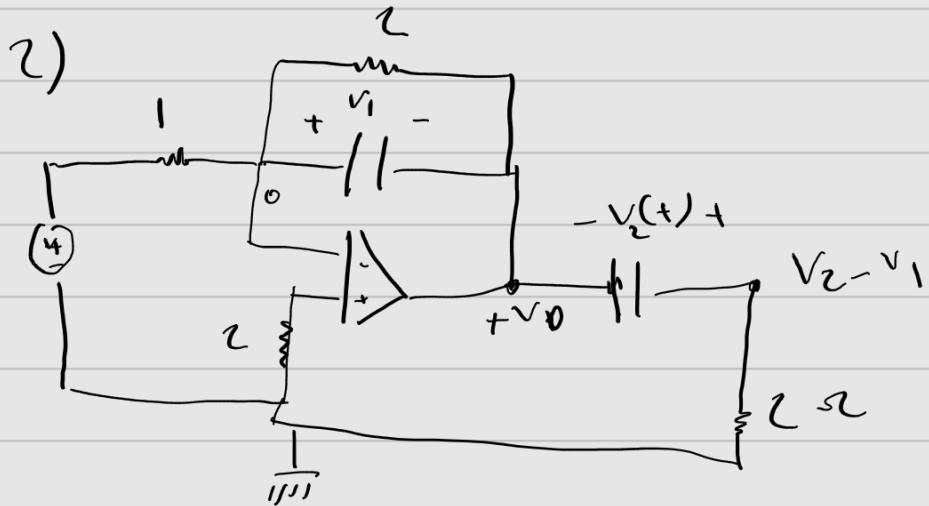
$$\rightarrow i_{SC} = \frac{V_i}{1k} = -\frac{V_{S1}}{2}$$



① in

$$V_D = -V_1$$

$$V_1 = \frac{V_S}{D + \frac{1}{Z}}$$

$\mu CL$

$$\text{I)} \frac{-V_S}{1} + \frac{V_1}{Z} + \frac{dV_1}{dt} = 0 \rightarrow \boxed{\frac{dV_1}{dt} + \frac{V_1}{Z} = V_S(t)}$$

$$\text{II)} \frac{V_2 - V_1}{Z} = \frac{dV_2}{dt} \rightarrow -Z \frac{dV_2}{dt} = V_2 - V_1$$

$$Z \frac{dV_2}{dt} = +\frac{V_S}{D + \frac{1}{Z}} - V_2$$

$$\rightarrow Z \frac{dV_2}{dt} + V_2 = t \frac{\sqrt{S}}{D + \frac{1}{Z}}$$

$$\Rightarrow \left( Z^2 D + 1 \right) \left( D + \frac{1}{Z} \right)^{-1} V_2 = \sqrt{S}$$

$$(Z^2 D^2 + Z D + \frac{1}{Z}) V_2 = \sqrt{S}$$

$$\boxed{\frac{Z^2 D^2}{\sqrt{S}} V_2 + \frac{Z D}{\sqrt{S}} V_2 + \frac{1}{Z} V_2 = \sqrt{S}}$$

اگر فرض کنیں خردی انتفاع ہے اس عبارت ایفرا نسل بھارت پر:


$$|V_0| = 15 \quad \text{و} \quad V_0 = 15$$

لیے جائیں  
بانی  
مشکل  
نہیں

$$\frac{dV_1}{dt} + \frac{V_1}{2} + V_- - V_S = 0 \quad \left\{ \begin{array}{l} \rightarrow \frac{dV_1}{dt} + \frac{3}{2} V_1 = V_S - 15 \\ \frac{2dV_2}{dt} + V_2 + 15 = 0 \end{array} \right.$$

$$V_0 = -15$$
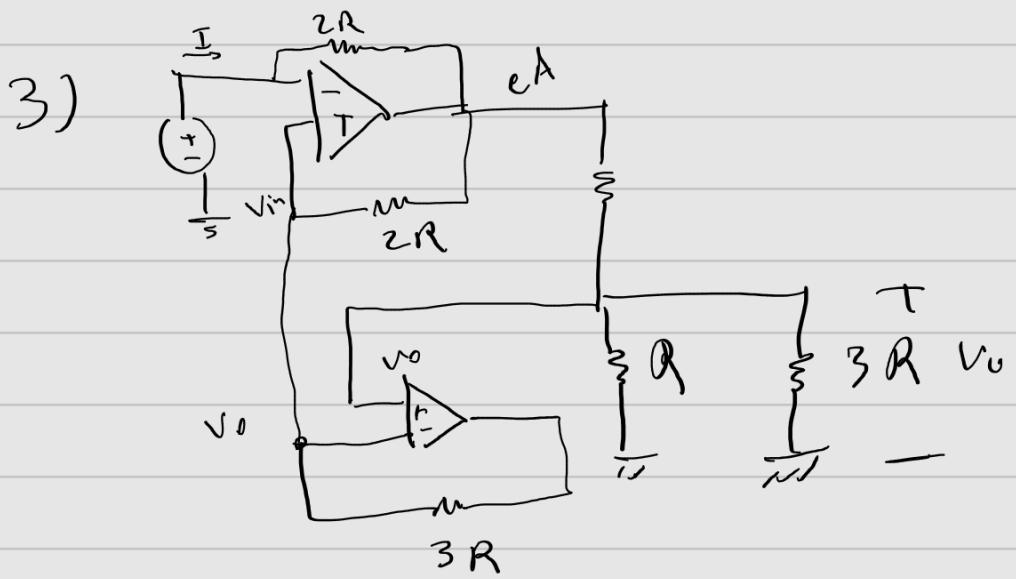
$$\frac{dV_1}{dt} + \frac{3}{2} V_1 = V_S + 15$$
$$\frac{2dV_2}{dt} + V_2 - 15 = 0$$



$$V_o = V_{in} \rightarrow A_v = \frac{V_o}{V_{in}} = 1 \rightarrow I = \text{const}$$

*R ist definiert*

$$R_{in} = \frac{V_{in}}{I_{in}}$$

$$\frac{V_{in} - eA}{2R} = I$$

$$\text{KCL: } \frac{V_o - eA}{R} + \frac{V_o}{\frac{3R}{4}} = 0 \rightarrow eA = \frac{4}{3}V_o + V_o \xrightarrow{V_o = V_{in}}$$


$$2RI = V_{in} - eA = -\frac{4}{3}V_o$$

$$\rightarrow R_{in} = -\frac{2}{3}V_{in} \rightarrow R_{in} = \frac{V_{in}}{I_{in}} = -\frac{3}{2}R$$


*jedes Ergebnis*

$$\begin{aligned} V_1 &= \sin(\tau) \\ V_2 &= \cos(\tau) \end{aligned} \quad \left\{ \begin{array}{l} \text{باي خربه تند} \\ \text{درست} \end{array} \right.$$

(4)

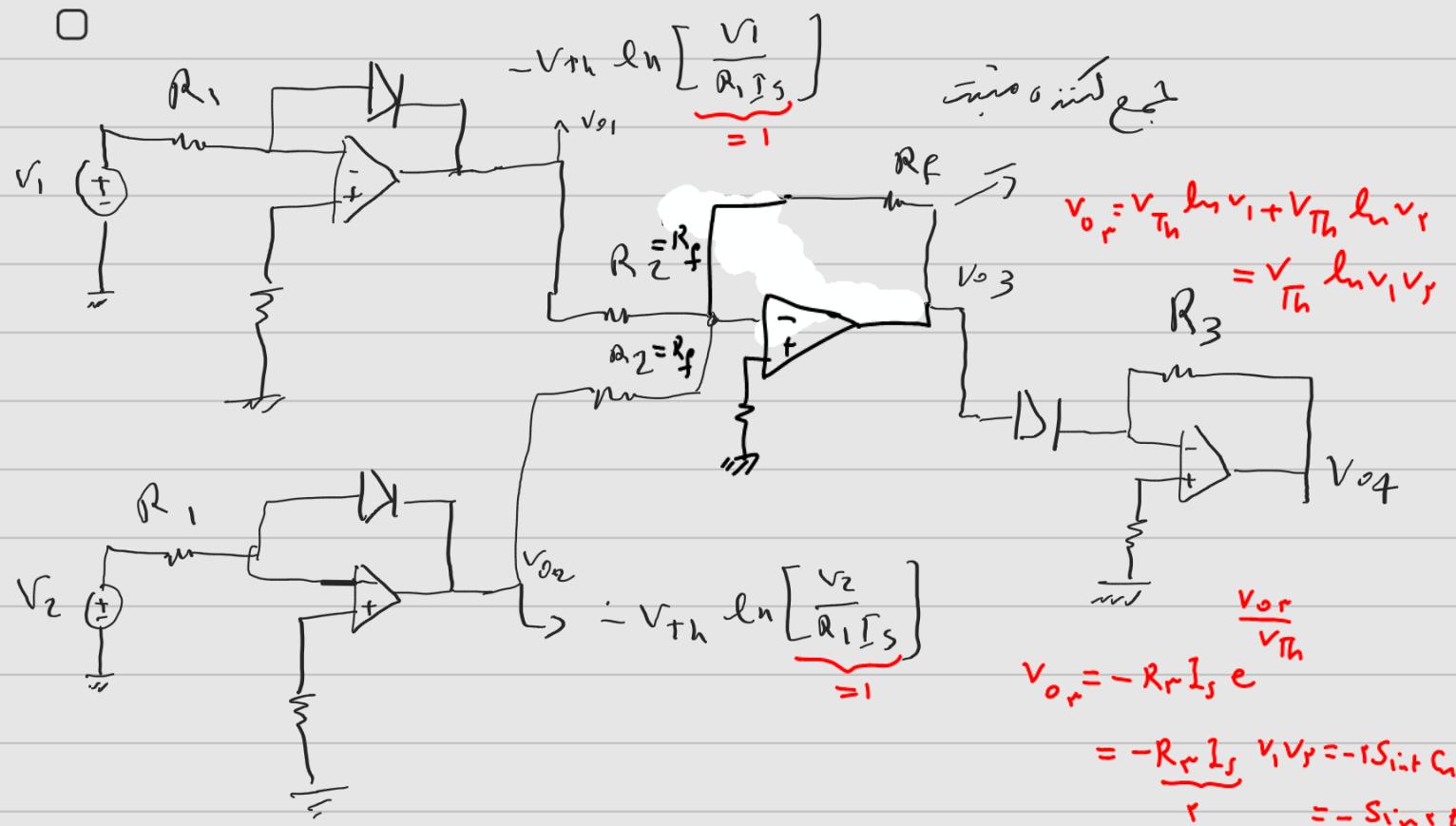
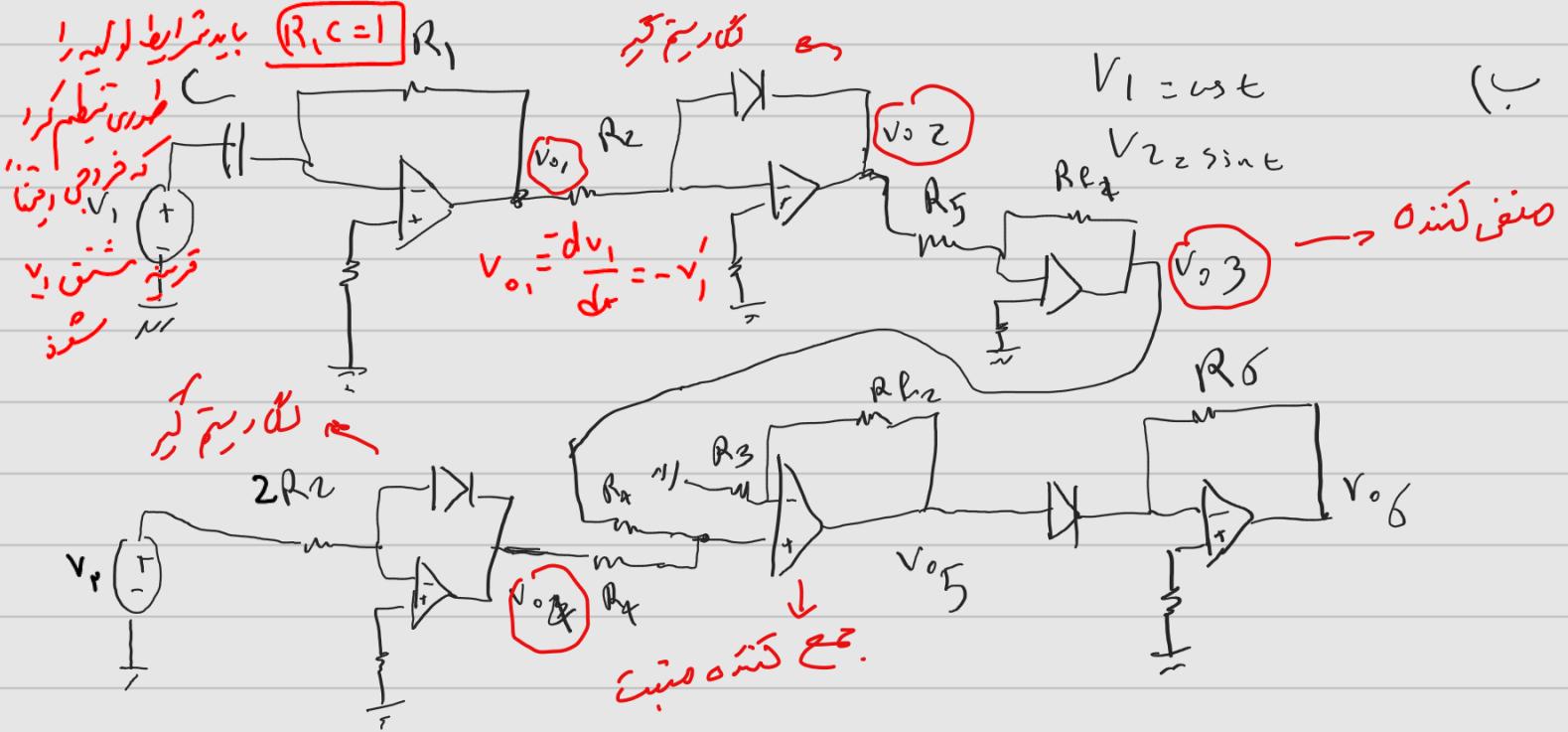
$$\rightarrow V_{oq} = -\sin(zt) \rightarrow \boxed{V_{oq} = \sin rt}$$



$$R_1 C = 1$$

$$R_{F1} = R_5$$

$$V_{o2} = -V_{Th} \ln \left[ \frac{-V_1}{R_2 I_s} \right]$$

$$R_{F2} = R_3$$

$$V_{o3} = V_{Th} \ln \left[ \frac{-V_1}{R_2 I_s} \right]$$

$$V_{o5} = \left( 1 + \frac{R_{F2}}{R_3} \right) \times \frac{1}{2} (V_{o3} + V_{o4})$$

$$= 2 \times \frac{1}{2} V_{Th} \left[ \ln \left( \frac{-V_1}{R_2 I_s} \right) - \ln \left( \frac{V_2}{2R_2 I_s} \right) \right]$$

$$V_{o4} = -V_{Th} \ln \left[ \frac{V_2}{2R_2 I_s} \right]$$

$$= V_{Th} \ln \frac{-2V_1}{V_p}$$

$$V_{o6} = -R_6 I_s e^{\frac{V_5}{V_{Th}}} = -2 R_6 I_s$$

$$= V_{Th} \ln \frac{-2(-\sin t)}{\sin t}$$

$$= V_{Th} \ln 2$$



$$-2 R_6 I_s = \text{درجه حراري}$$

نهاده اين رعایل بیشتر سیزده تقریباً

در شرط هر دوی هم ممکن است


اپنے بیکار انتگرال کر اسٹرائی مدار را کریں ۵
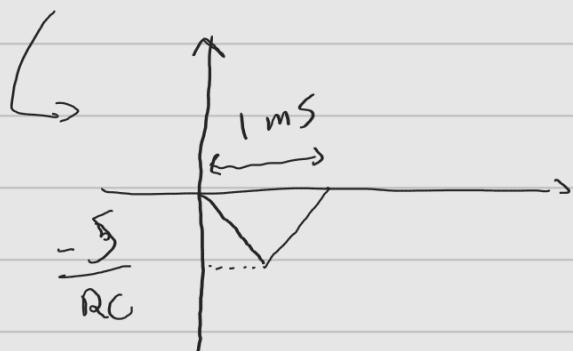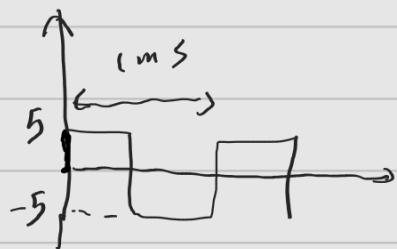
$$= -\frac{1}{RC} \int_0^t v_s(\lambda) d\lambda$$



$$\frac{5}{RC} = 10$$


$$RC = \frac{1}{2}$$

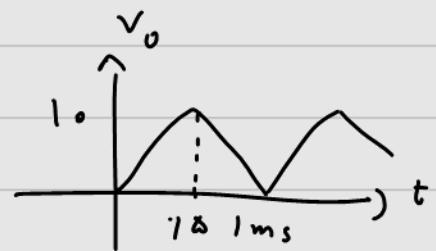

$$\left\{ \begin{array}{l} R = 10k \\ C = 50 \mu F \end{array} \right. \rightarrow$$

$$RC = \frac{1}{2}$$

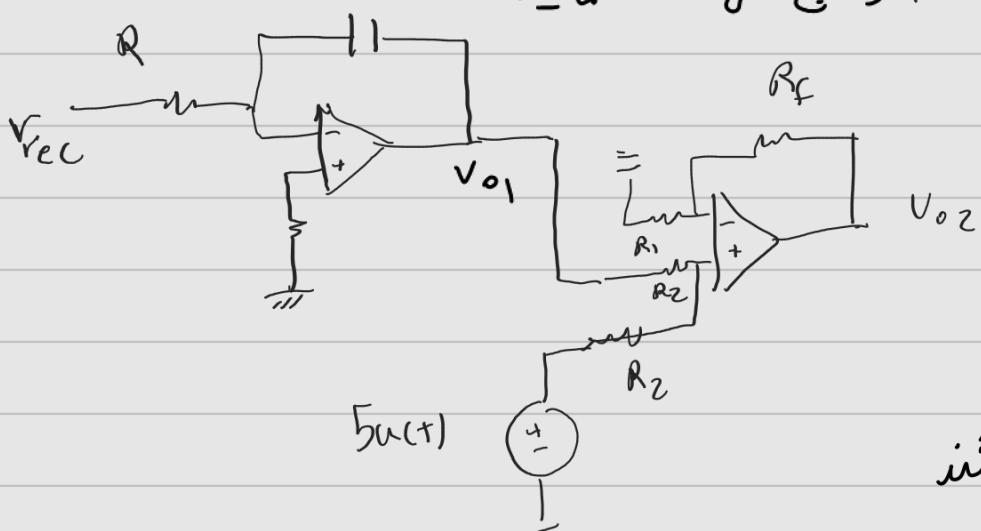اگر نیہ بارہ تینیت کندہ سفی باہر ۱۰  
ضہبکم کر کر جو تینی پست بارانہ زار لیں مزدوج  
و اگر بیکار ۵ و تجھے کم کر کر جو شش بارانہ دلت  
ترکیب ہے۔



هر کون عدد لئے کہ سروچ کند  
قابل قبول اسے

$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) \times \frac{R_2}{R_2 + R_2} (v_1 + v_2)$$

$$R_f = R_1$$

